

Second order circuits:

- If $\omega_0^2 < 0 \rightarrow$ system is not stable
- Over-d: $\zeta > 1$; Critically-d: $\zeta = 1$; Under-d: $0 < \zeta < 1$
- If capacitance $\rightarrow \infty$ - capacitor can be ignored (shortened)
- If current source = 0, it is actually disconnected

Singularity functions:

- $\int_a^b \varphi(\lambda) \delta(\lambda - t_0) = \int_a^b \varphi(t_0) \delta(\lambda - t_0) = \begin{cases} \varphi(t_0) & a < t_0 < b \\ 0 & \text{else} \end{cases}$
- $\delta_{-1}(t) = u(t)$; $\delta_{-2}(t) = r(t) = tu(t)$
- $P_\Delta(t) = (u(t) - (u(t - \Delta)) \frac{1}{\Delta}$

Laplace Transform:

- Constant's behavior: Same behavior as for constants inside integrals.
- Laplace of 1 is same as Laplace of step function
- $L^{-1}[F(s) \cdot e^{as}] = L^{-1}[F(s)]$ time shifted by $\alpha = f(t + \alpha)$
- Definition (unilateral Laplace transform) : $F(s) = \int_0^\infty f(t) e^{-st} dt$
- $s = j\omega$ in the Laplace domain
- Initial Value Theorem: $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$
- Final Value Theorem: $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$
- Integration: $L\{\int_0^t f(\tau) d\tau\} = \frac{1}{s} F(s)$
- Time shift: $L\{f(t - \tau)\} = e^{-s\tau} F(s)$
- Frequency shift: $L\{e^{-at} f(t)\} = F(s + a)$
- Time Scaling: $L\{f(\frac{t}{a})\} = aF(as)$
- Frequency Scaling: $L\{af(at)\} = F(\frac{s}{a})$
- Differentiation in time: $L\{f^{(n)}(t)\} = s^n F(s) - s^{n-1} f(0^-) - s^{n-2} f^{(1)}(0^-) - \dots - f^{(n-1)}(0^-)$

$$L\{f^{(n)}(t)\} = s^n F(s) - s^{n-1} f(0^-) - s^{n-2} f^{(1)}(0^-) - \dots - f^{(n-1)}(0^-)$$

Solving ODE with Laplace transform:

- Transform of a differential equation: $Y(s) = U(s) \frac{P_2(s)}{P_1(s)} - \frac{Q_1(s)}{Q_2(s)}$
- The term $G(s) = \frac{P_2(s)}{P_1(s)} = \frac{\text{output}}{\text{input}}$ is called the transfer function.
- The response to the input is $Y(s) = \frac{P_2(s)}{P_1(s)} U(s) = G(s) U(s)$
- Transfer function: For continuous-time input signal $U(s)$ and output $Y(s)$, the transfer function $G(s)$ is the linear mapping of the Laplace transform of the input $U(s) = \mathcal{L}\{u(t)\}$ to the Laplace transform of the output $Y(s) = \mathcal{L}\{y(t)\}$ such that $Y(s) = G(s) U(s)$
- Transfer function = Laplace transform of the impulse response of an LTI system when initial conditions = 0
- For a sinusoidal steady state source: $V_s(\text{or } I_s) = A \sin(\omega t)$, the output would be $A |G(s)| \cdot \sin\left(\omega t + \angle G(s)\right)$

Convolution:

- Define "impulse response" : if $x(t) = \delta(t)$, then $y(t) = h(t)$ is the impulse response. General solution would be $y_{total} = ZIR + convolution$
- The convolution integral: $y(t) = x(t) * h(t) = \int_{-\infty}^\infty x(\tau) h(t - \tau) d\tau = \int_{-\infty}^\infty x(t - \tau) h(\tau) d\tau$
- $h(\tau)$ May be nonzero only at $\tau > 0$, $h(t - \tau)$ can be nonzero for $t - \tau > 0$. Updated lims: $y(t) = x(t) * h(t) = \int_0^t x(\tau) h(t - \tau) d\tau = \int_0^\infty x(t - \tau) h(\tau) d\tau$
- Impulse starting at $t = 0$, $y(t) = x(t) * h(t) = \int_0^t x(\tau) h(t - \tau) d\tau = \int_0^\infty x(t - \tau) h(\tau) d\tau$
- Properties:

- $x * h = h * x$
- $(g + h) * x = g * x + h * x$
- $(h * x)' = h' * x = h * x'$ (assuming derivative exists)
- $x(t) * \delta(t) = x(t)$
- Time shift: if $y(t) = x(t) * h(t) \Rightarrow x(t) * h(t - t_0) = y(t - t_0)$
- Specific case: if $h(t) = \delta(t - t_0) \Rightarrow x(t) * h(t) = x(t - t_0)$
- $x(t) * \delta'(t) = x'(t) * \delta(t) = x'(t)$

Phasors & Sinusoidal Steady State:

- Sinusoidal Steady State: a state of a system with a sine input, "after a long time has passed", i.e. all Transient effects are gone.
- It will be more convenient to work with complex numbers: $A_m \cos(\omega t + \varphi) = \text{Re}[A_m e^{j(\omega t + \varphi)}] = \text{Re}[A_m e^{j\varphi} e^{j\omega t}]$
- Define the Phasor as: $\tilde{A} \equiv A_m e^{j\varphi} \Rightarrow A_m \cos(\omega t + \varphi) = \text{Re}[\tilde{A} e^{j\omega t}]$
- Transforming differential equations into algebraic equations: $\frac{d^n}{dt^n} (A_m \cos(\omega t + \varphi)) = \frac{d^n}{dt^n} (\text{Re}[\tilde{A} e^{j\omega t}]) = (\text{Re}[(j\omega)^n \tilde{A} e^{j\omega t}])$
- Kirchhoff's laws apply for Phasors as well

- Alternate notation: $\tilde{A} \angle \varphi$
- If $\text{Re}[s] < 0 \rightarrow$ system is not stable, otherwise \rightarrow stable
- If feedback: $H_{new} = \frac{G(s)}{G(s) \pm 1}$, (where \pm = sign of feedback signal??)

Impedance/Admittance:

- Impedance: the ratio of the voltage and the current. For sinusoidal signals: $Z_x = \frac{V_x}{I_x}$, Admittance: $Y_x = \frac{I_x}{V_x}$
- Since $Z_x \tilde{I}_x = \tilde{V}_x$, the voltage and current might have different phases
 - For an Inductor, current lags behind voltage by $\frac{\pi}{2}$, for capacitors it's the other way around.
- In Sinusoidal steady state, each component can be treated as a "resistor" with R = impedance. Follows ohm's law (same for Phasors). Norton & Thevenin are legal.

Power in Sinusoidal Steady State:

- For sinusoidal steady state we have:
 - $V(t) = V_m \cos(\omega t + \angle V)$; $I(t) = I_m \cos(\omega t + \angle I)$
 - $P(t) = V_m I_m \cos(\omega t + \angle V) \cos(\omega t + \angle I) = \underbrace{\frac{1}{2} V_m I_m \cos(\angle V - \angle I)}_{\text{average power}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \angle V + \angle I)}_{\text{time dependent power at double frequency}}$

Coupled Inductors:

- Coupled inductors are such that a change in the current through one inductor results in a change of the voltage across the other.
- The coupling equations are given in formulae , M = mutual inductance
- Coupling coefficient is defined as: $k = \frac{|M|}{\sqrt{L_1 L_2}}$, $0 \leq k \leq 1$
 - $k = 0 \Rightarrow$ no coupling ; $k = 1 \Rightarrow$ full coupling
- At Sinusoidal Steady State we have $\begin{cases} \tilde{V}_1 = j\omega L_1 \tilde{I}_1 + j\omega M \tilde{I}_2 \\ \tilde{V}_2 = j\omega M \tilde{I}_1 + j\omega L_2 \tilde{I}_2 \end{cases}$

Ideal Transformers:

- Idealization assumptions: No energy dissipation, No flux leakage $\Rightarrow k = 1$ (full coupling), Infinite inductance: $L_1, L_2, M \rightarrow \infty$
- Ideal transformer is LTI.
- Since there is no power loss, any power entering on one side will emanate from the other: $V_1(t) I_1(t) + V_2(t) I_2(t) = 0$
- Ideal transformers different dots: $\frac{v_1}{v_2} = -\frac{n_1}{n_2} \frac{i_1}{i_2} = \frac{n_2}{n_1}$

Reflection:

- Primary: the segment with a steady state input
- Secondary: the other inductor's segment
- Reflection process: Usually reflect secondary onto primary. If the opposite reflection is desired, n_1, n_2 switch places in all reflections. New circuit is w/o the coupled inductors and is connected at those inductors' terminals.
- If Circuit is in SSS, $V = RI = ZI$ where Z is SSS condition (impedance)

Dependent sources:

Diagram	Name	Case Identifiers	Formula for the Unknown
	Current controlled Current source	$I_2 = \alpha I_1$ $V_1 = 0$	Current Ratio: $\alpha = \frac{I_2}{I_1}$
	Voltage controlled Current source	$I_1 = 0$ $I_2 = g_m V_1$	Transfer Conductance: $g_m = \frac{I_2}{V_1}$
	Current controlled Voltage source	$V_1 = 0$ $V_2 = r_m I_1$	Transfer Resistance: $r_m = \frac{V_2}{I_1}$
	Voltage controlled Voltage source	$I_1 = 0$ $V_2 = \mu V_1$	Voltage Ratio: $\mu = \frac{V_2}{V_1}$

- The sources are active. They may amplify the current/voltage/power
- Controlled sources may not be zeroed. While using superposition/Norton/Thevenin equivalents, only independent sources are zeroed.

Translational Mechanical Systems:

	Mechanical	Electrical
Signals	V — velocity f — force	V — voltage I — current
Components	Viscous friction or linear dashpot with constant B, that obeys $v = \frac{1}{B} f$ Spring with constant K $v = \frac{1}{k} \frac{df}{dt}$ Mass (M) that obeys $f = M \frac{dv}{dt}$	Resistor that obeys $V = RI$ Inductor that obeys $V = L \frac{dI}{dt}$ Capacitor that satisfies $I = C \frac{dV}{dt}$
voltage of ground=0 (you can apply any current to grnd. and voltage remains 0)		velocity of ground=0 (you can apply any force to ground and voltage remains 0)

Rotational Mechanical Systems:

	Mechanical	Electrical
Signals	ω — velocity τ — torque	V — voltage I — current
Components	Torsional friction (B), $\omega = \frac{1}{B} \tau$ Torsional spring (K) $\omega = \frac{1}{k} \frac{d\tau}{dt}$ Moment of inertia (J) $\tau = J \frac{d\omega}{dt}$	Resistor that obeys $V = RI$ Inductor that obeys $V = L \frac{dI}{dt}$ Capacitor that satisfies $I = C \frac{dV}{dt}$

- If connected through velocity – parallel. If connected through force – series.

Electrical	Mechanical
$\sum_{node} \text{current} = 0$	$\sum_{object} \text{forces} = 0$

State space representation:

- The following set is called a state-space representation:

$$\begin{cases} \dot{\bar{x}}(t) = A\bar{x}(t) + \bar{b}u(t) \\ y(t) = \bar{c}\bar{x}(t) + du(t) \\ \bar{x}(t=0) \equiv \bar{x}(0) \end{cases}$$

$\bar{x}(t)$	State variable
$u(t)$	Input
$y(t)$	Output
A	Dynamic matrix
\bar{b}, \bar{c}, d	---

$$A = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 \\ 0 & 0 & 1 & & \\ \vdots & \vdots & & \ddots & \\ -a_0 & -a_1 & -a_2 & \dots & -a_{n-1} \end{bmatrix}, \bar{b} = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 1 \end{bmatrix}, \bar{c} = [b_0 \dots b_{n-1}], d = 0$$

$$\begin{pmatrix} x_1(0) \\ x_2(0) \\ \vdots \\ x_n(0) \end{pmatrix} = \begin{bmatrix} \bar{c} \\ \bar{c}A \\ \vdots \\ \bar{c}A^{n-1} \end{bmatrix}^{-1} \begin{pmatrix} y(0) \\ y^{(1)}(0) \\ \vdots \\ y^{(n-1)}(0) \end{pmatrix}$$

Where $a_0, a_1 \dots$ are coefficients of y when y^n is ordered by ascending n.

- In general case, where the input appears with derivatives, the ODE can be written as

$$y^{(n)}(t) + \sum_{k=0}^{n-1} a_k y^{(k)}(t) = \sum_{m=0}^{n-1} b_m u^{(m)}(t)$$

- Using linearity (or superposition), if we find the result of a simple input without derivatives $y_u(t)$, then the general solution is

$$y(t) = \sum_{m=0}^{n-1} b_m y_u^{(m)}(t)$$

- If the RHS of the ODE contains a $b_n u^{(n)}(t)$ term, then $d = 0$ changes to $d = b_n$, and \bar{c} changes to

$$\bar{c} = [b_0, b_1, \dots, b_{n-1}] + b_n[-a_0, -a_1, \dots, -a_{n-1}]$$

Equivalent representations:

- Given a certain state variable $\bar{x}(t)$, we can use a transformation T to obtain a different representation. We are interested in representations where \tilde{A} is diagonal (assuming A has distinct eigenvalues)

- Steps to find a diagonal representation:

1. Find the eigenvalues of A by $\det(\lambda I - A) = 0$

2. Find the eigenvectors of A by solving eq-n set $(\lambda_k I - A)\bar{u}_k = 0$

a. If Eigenvector can't be found due to 2 unknowns and 1 eq. express \bar{u}_k as the same component (eg. $\bar{u}_k = \begin{bmatrix} u_{k2} \\ u_{k2} \end{bmatrix}$) and factor out the component. The result is the basis of all eigenvectors of the eigenvalue.

b. If a component of the eigenvector is independent, then it can be any value, but we select it to be 1 since that would be a basis for any other eigenvector of this eigenvalue.

3. Transformation matrix - eigenvectors as columns $T = [u_1 \ u_2 \ \dots \ u_n]$

4. Calculate the inverse matrix T^{-1} .

a. Matrix inverse 2x2: $\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$

b. Matrix inverse 3x3:

$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix}^{-1} = \frac{1}{a(ei-fh)-b(di-fg)+c(dh-eg)} \begin{bmatrix} ei-fh & -(bi-ch) & bf-ce \\ -(di-fg) & ai-cg & -(af-cd) \\ dh-eg & -(ah-bg) & ae-bd \end{bmatrix}$$

5. Find the new representation, eg. $\tilde{A} \equiv \Lambda = T^{-1}AT = \begin{bmatrix} \lambda_1 & & \\ & \ddots & \\ & & \lambda_n \end{bmatrix}$

State space Time Domain solution:

Given a system $\begin{cases} \dot{\bar{x}}(t) = A\bar{x}(t) + \bar{b}u(t) \\ y(t) = \bar{c}\bar{x}(t) \end{cases}$, we would like to find an expression for $\bar{x}(t)$ and through that we find $y(t)$.

(Input response?) $\bar{x}(t)$ consists of 2 parts: $\bar{x}(t) = \bar{x}_i(t) + \bar{x}_u(t)$, where:

o $\bar{x}_i = \Phi(t)\bar{x}(0)$ is the homogenous solution (ZIR)

o $\bar{x}_u = \int_0^t \Phi(t-\tau)\bar{b}u(\tau)d\tau$ is the response to the input (ZSR)

The matrix $\Phi(t) = e^{At}$ is called the transition/transfer matrix

We can express e^{At} by finding the diagonalizing transform:

$$\Lambda, T, T^{-1}, \Phi(t) = e^{At} = Te^{\Lambda t}T^{-1}, e^{\Lambda t} = \begin{bmatrix} e^{\lambda_1 t} & & \\ & \ddots & \\ & & e^{\lambda_n t} \end{bmatrix}$$

- Properties of matrix exponent:

o For $t = 0, e^{A0} = I$ (identity matrix)

$$\frac{d\Phi(t)}{dt} = Ae^{At} \quad e^{ax}e^{bx} = e^{(a+b)x} \quad e^X e^{-X} = I$$

o If matrices obey $XY=YX$. Then $e^X e^Y = e^Y e^X = e^{Y+X}$

State space Laplace Domain solution:

- Use Laplace Transforms to solve state-space equations:

$$\begin{aligned} L\{\dot{\bar{x}}(t) = A\bar{x}(t) + \bar{b}u(t)\} &\Rightarrow s\bar{x}(s) - \bar{x}(0) = A\bar{x}(s) + \bar{b}U(s) \\ &\Rightarrow (sI - A)\bar{x}(s) = \bar{x}(0) + \bar{b}U(s) \Rightarrow \bar{x}(s) \\ &= (sI - A)^{-1}\bar{x}(0) + (sI - A)^{-1}\bar{b}U(s) \end{aligned}$$

- Now, using $\bar{x}(s)$ we can find $\bar{Y}(s)$ using the row vector \bar{c} and adding $dU(t)$ if $d \neq 0$:

$$Y(s) = \bar{c}(sI - A)^{-1}\bar{x}(0) + \bar{c}(sI - A)^{-1}\bar{b}U(s) + dU(s)$$

OR:

$$Y(s) = \bar{c}(sI - A)^{-1}\bar{x}(0) + G(s)U(s)$$

- The transfer function is $\left(\frac{\text{output}}{\text{input}}, 0 \text{ init. Cond.}\right)$

$$G(s) = \frac{Y(s)}{U(s)} = \bar{c}(sI - A)^{-1}\bar{b} + d$$

- $L\{e^{At}\} = (sI - A)^{-1}$

Diagonal representation:

o In the case that the transfer function $G(s)$ has distinct poles, we can expand it as: $G(s) = p_0 + \frac{p_1}{s-s_1} + \frac{p_2}{s-s_2} + \dots + \frac{p_n}{s-s_n}$. Then a diagonal

representation $\{A, \bar{b}, \bar{c}, d\}$, is given by: $A = \begin{bmatrix} s_1 & & 0 \\ & \ddots & \\ 0 & & s_n \end{bmatrix}; \bar{b} = \begin{bmatrix} b_1 \\ \vdots \\ b_n \end{bmatrix}$

$$\bar{c} = [c_1 \dots c_n]; d = p_0; \bar{x}_0 = \begin{bmatrix} \bar{c} \\ \bar{c}A \\ \vdots \\ \bar{c}A^{n-1} \end{bmatrix}^{-1} \bar{y}(0) \quad \forall \text{ pairs } c_i, b_i, \text{ s.t. } c_i \cdot d_i = p_i \text{ ascend.n.}$$

- Two (of many) legitimate choices are:

$$\bar{b} = \begin{bmatrix} 1 \\ \vdots \\ 1 \end{bmatrix}; \bar{c} = [p_1 \dots p_n] \quad \bar{b} = \begin{bmatrix} p_1 \\ \vdots \\ p_n \end{bmatrix}; \bar{c} = [1 \dots 1] \leftarrow \text{canonical form}$$

Frequency response and resonance:

- For a transfer function $G(s)$ and an input $A \sin(\omega t)$, the output is: $y_{ss}(t) = A|G(j\omega)| \sin(\omega t + \arg G(j\omega))$
- Transfer function is sometimes denoted as H instead of G .
- Since the Amplitude and phase depend on the frequency, we get a different response for each frequency
- Resonance Frequency: The frequency for which the voltage and current supplied to the circuit have the same phase. Denote as ω_0 .


Bode Plots:

- dB = $20 \log(x)$
- DC Gain means 0 frequency: $\omega = 0$
- Real Gain: $= 20 \log(|Q(s)|) - 20 \log(|P(s)|)$ where $G(s) = \frac{Q(s)}{P(s)}$
- Diff between real & asymptotic gain: $|G(s)|$
- Cutoff frequency: Where the gain is 0dB (when Bode plot intersects x-axis)
- Bode plot slope: $\frac{G(\omega_2) - G(\omega_1)}{\log(\omega_2) - \log(\omega_1)} \left[\frac{\text{dB}}{\text{dec}} \right]$
- If magnitude Bode plot doesn't start from the y-axis, unless stated otherwise assume that it comes from a very high/low value, then we have a zero/pole at the origin of order corresponding to the slope.
- Minimal phase: All poles & zeros are in the left side of the complex plane.
- Logarithm: $\log_b a = c \Leftrightarrow b^c = a$

Difference between exact and asymptotic value @ the cutoff frequency

Simple Zero	+3[dB]
Simple Pole	-3[dB]
Conjugate pair of Zeroes	$-20 \log_{10} \left(\frac{1}{2 \zeta } \right)$
Conjugate pair of Poles	$+20 \log_{10} \left(\frac{1}{2 \zeta } \right)$

Circuits' analysis summary:

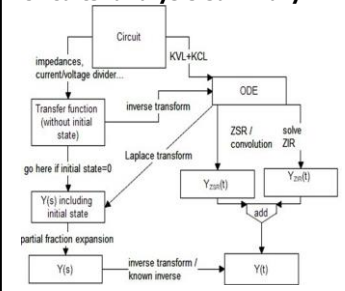

Filters:

